

TWO PORT NETWORKS – h-PARAMETER BJT MODEL

The circuit of the basic two port network is shown on the right. Depending on the application, it may be used in a number of different ways to develop different models. We will use it to develop the h-parameter model. Other models may be covered in EE III.

The h-parameter model is typically suited to transistor circuit modeling. It is important because:

1. its values are used on specification sheets
2. it is one model that may be used to analyze circuit behavior
3. it may be used to form the basis of a more accurate transistor model

The h parameter model has values that are complex numbers that vary as a function of:

1. Frequency
2. Ambient temperature
3. Q-Point

The revised two port network for the h-parameter model is shown on the right.

At low and mid-band frequencies, the h-parameter values are real values. Other models exist because this model is not suited for circuit analysis at high frequencies.

The h-parameter model is defined by:

$$\begin{vmatrix} V_1 \\ I_2 \end{vmatrix} = \begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} \begin{vmatrix} I_1 \\ V_2 \end{vmatrix}$$

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad (\text{KVL})$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad (\text{KCL})$$

The h-parameter model for the common emitter circuit is on the right. On spec sheet:

$$h_{11} = h_{ix}$$

$$h_{12} = h_{rx}$$

$$h_{21} = h_{fx}$$

$$h_{22} = h_{ox}$$

h_{rx} and h_{fx} are dimensionless ratios

h_{ix} is an impedance $\langle \Omega \rangle$




h_{ox} is an admittance $\langle S \rangle$

where x = lead based on circuit configuration

e = emitter for common emitter

c = collector for common collector

b = base for common base

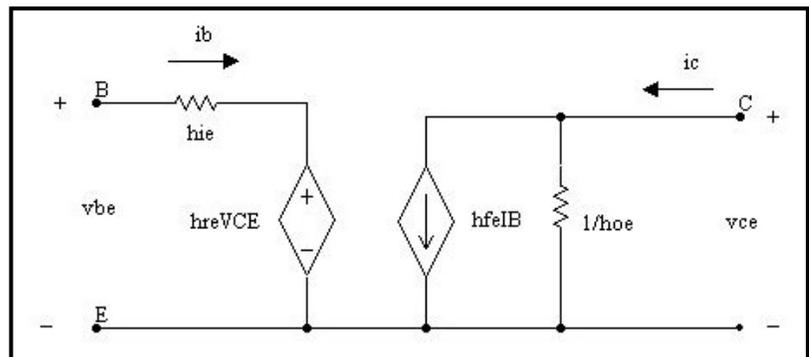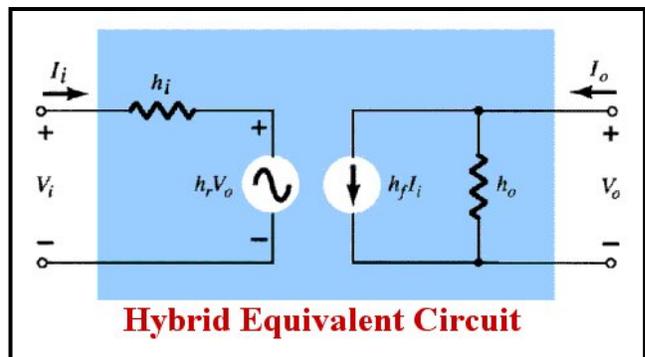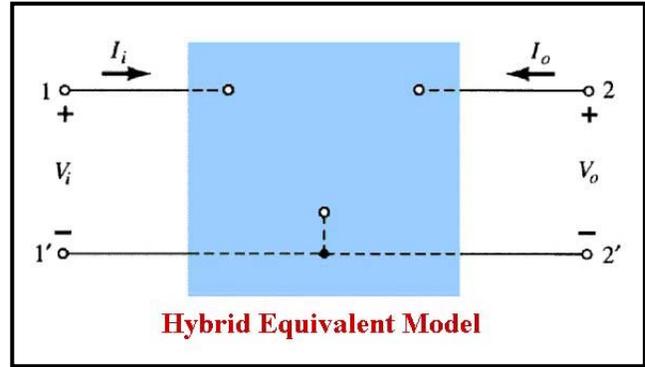


TWO PORT NETWORKS – h-PARAMETER BJT MODEL

Short Circuit Input Impedance

$h_{11} = Z_{IN}$ with output shorted $\langle \Omega \rangle$

$$h_{11} = \left. \frac{V_i}{I_i} \right|_{V_o = 0}$$

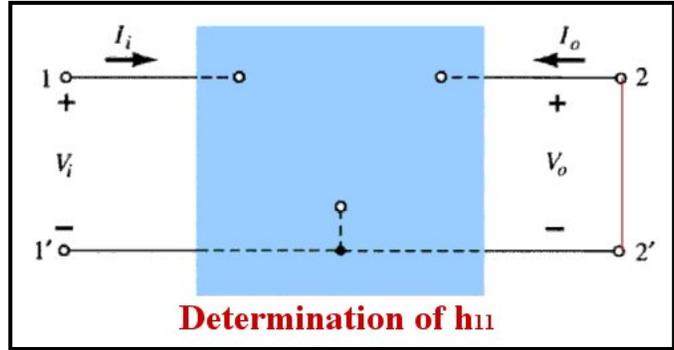1. Short terminals 2 2'
2. Apply test source V_i to terminal 1 1'
3. Measure I_i
4. Calculate h_{11}




Open Circuit Reverse Transfer Ratio

h_{12} <dimensionless>

$$h_{12} = \left. \frac{V_i}{V_o} \right|_{I_i = 0}$$

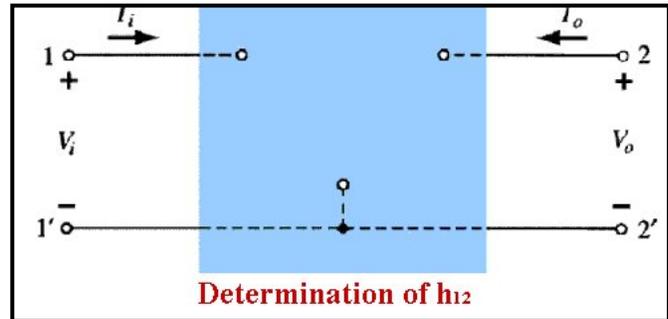1. Open terminals 1 1'
2. Apply test source V_2 to terminal 2 2'
3. Measure V_i
4. Measure V_o
5. Calculate h_{12}




Short Circuit Forward Transfer Ratio

h_{21} = <dimensionless>

$$h_{21} = \left. \frac{I_o}{I_i} \right|_{V_o = 0}$$

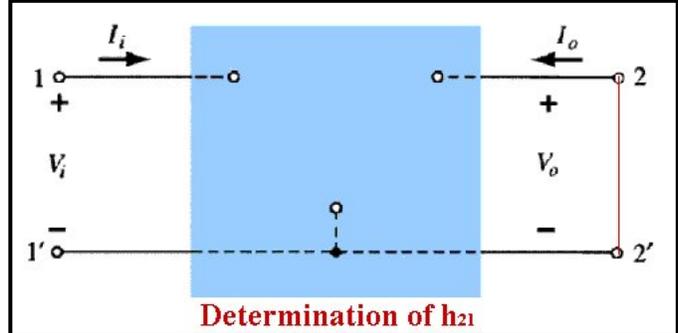1. Short terminals 2 2'
2. Apply test source V_i to terminal 1 1'
3. Measure I_i
4. Measure I_o
5. Calculate h_{21}




Open Circuit Output Admittance

h_{22} <Siemens>

$$h_{22} = \left. \frac{I_o}{V_o} \right|_{I_i = 0}$$

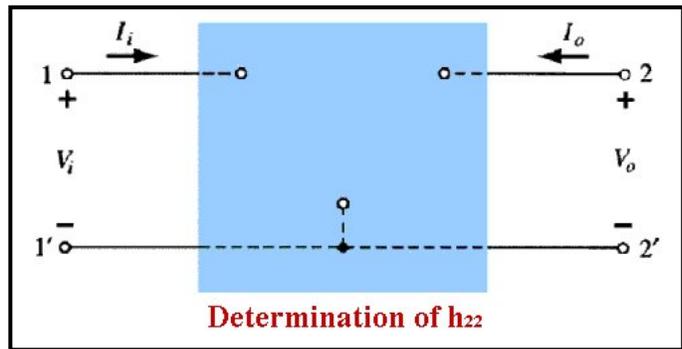
1. Open terminals 1 1'
2. Apply test source V_2 to terminal 2 2'
3. Measure I_o
4. Measure V_o
5. Calculate h_{22}



BJT Hybrid Model π

Hybrid Model π

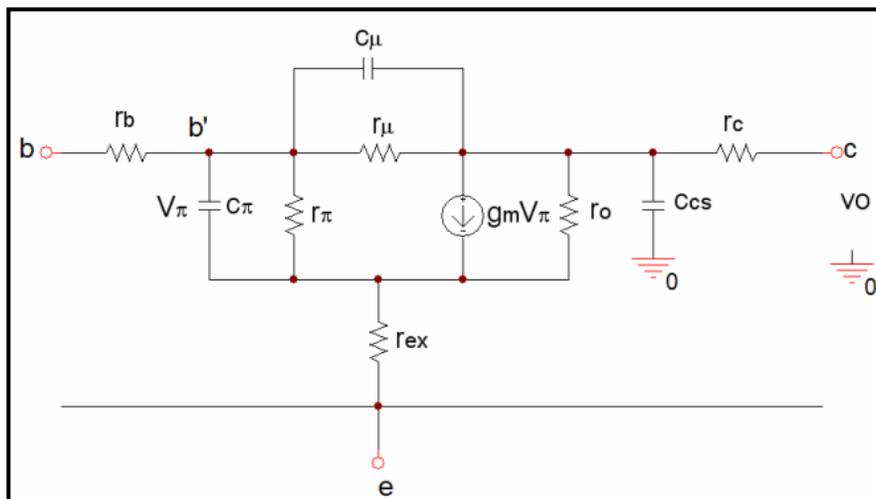All frequencies
 Better model than h parameter model since it contains frequency sensitive components.
 These are ac small signal parameters which are determined at the Q point



Parasitic Resistances

$r_b = r_{b'e} =$ ohmic

resistance –
 voltage drop in

base region caused by transverse flow of majority carriers, $50 \leq r_b \leq 500$

$r_c = r_{ce} =$ collector emitter resistance – change in I_c due to change in V_c , $20 \leq r_c \leq 500$

$r_{ex} =$ emitter lead resistance – important if I_c very large, $1 \leq r_{ex} \leq 3$

Parasitic Capacitances

$C_{je0} =$ Base-emitter junction (depletion layer) capacitance, $0.1 \text{pF} \leq C_{je0} \leq 1 \text{pF}$

$C_{\mu0} =$ Base-collector junction capacitance, $0.2 \text{pF} \leq C_{\mu0} \leq 1 \text{pF}$

$C_{cs0} =$ Collector-substrate capacitance, $1 \text{pF} \leq C_{cs0} \leq 3 \text{pF}$

$C_{je} = 2C_{je0}$ (typical)

$\psi_0 = .55 \text{V}$ (typical)

$\tau_F =$ Forward transit time of minority carriers, average of lifetime of holes and electrons, $0 \text{ps} \leq \tau_F \leq 530 \text{ps}$

$C_b =$

$$C_{\mu} = \frac{C_{\mu0}}{\sqrt{1 + \frac{V_{cb}}{\psi_0}}}$$

$$C_{cs} = \frac{C_{cs0}}{\sqrt{1 + \frac{V_{cs}}{\psi_0}}}$$

$$C_b = \tau_F g_m$$

Hybrid Model Pi Parameters

$r_{\pi} = r_{b'e} =$ dynamic emitter resistance – magnitude varies to give correct low frequency value of $V_{b'e}$ for I_b

$r_{\mu} = r_{b'c} =$ collector base resistance – accounts for change in recombination component of I_b due to change in V_c which causes a change in base storage

$c_{\pi} = C_{b'e} =$ dynamic emitter capacitance – due to $V_{b'e}$ stored charge

$c_{\mu} = C_{b'c} =$ collector base transition capacitance (C_{TC}) plus Diffusion capacitance (C_d) due to base width modulation

$g_m V_{\pi} = g_m V_{b'e} = I_c =$ equivalent current generator

BJT Hybrid Model π

$$g_m = \frac{I_C}{V_T}$$

$$V_T = \frac{k T}{q} = 26\text{mV @ } 300^\circ\text{K}$$

$$g_m = \frac{I_C}{26\text{mV}}$$

$$r_\pi = \frac{(26\text{mV})(\beta)}{I_C} = \frac{26\text{mV}}{I_B}$$

$$\beta = g_m r_\pi$$

$$i_c = \frac{\beta v_\pi}{r_\pi} = g_m v_\pi$$

$$r_o = \frac{V_A}{I_C} \quad \text{where } 50 \leq V_A \leq 100$$

f_T = Gain Bandwidth Product (spec sheet is 300MHz)

C_μ corresponds approximately to C_{OBO} (on spec sheet is 8pF for 2N2222A)

τ_{CB} = collector base time constant (spec sheet is 150ps for 2N2222A)

$$r_b = \frac{\tau_{CB}}{C_\mu}$$

$$C_\pi = \frac{\beta}{2 \pi r_\pi f_T} - C_\mu$$

Low and Midband Frequency Hybrid Model π

At low frequencies, all X_c for hybrid model π are very large. Since they are in parallel with a much lower than their associated resistances, the X_c component may be ignored (replace with an open). At frequencies over a few 100kHz, they must be considered. At high frequencies, they shunt (short) the parallel resistances.


r_μ is very large and may be ignored (replace with an open)

r_b is much smaller than r_π . Since they are in series, r_b is often ignored (replaced with a short or lumped with r_π) since the current, I_B the current through both, is also very small.

r_{ex} is very small and is often ignored (replace with a short) unless I_E is very large.

r_o is very large and may be ignored at low frequencies

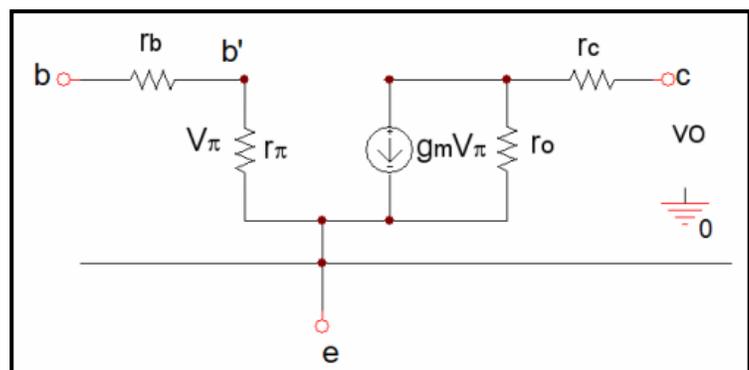$i_c = i_o \cong g_m v_\pi$ (where $v_{b'e} = v_\pi$)



BJT Hybrid Model π

High Frequency Model

f_i transition frequency due to parasitic capacitances

Apply i_{in} , and short the output

Ignore the following parameters:


$r_b = \text{small}$

$r_{ex} = \text{very small}$

$r_{\mu} = \text{very large}$

$r_c \ll r_o$ Since they are in parallel, ignore r_o

X_{CCS}

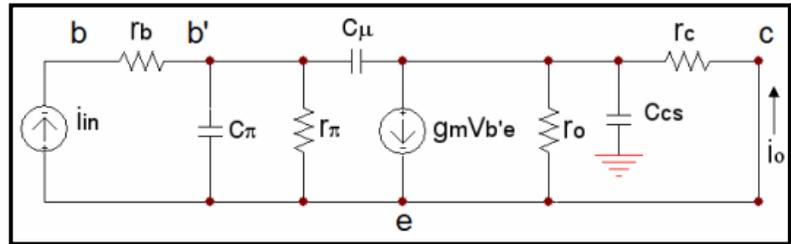

In the text and the following, s and $j\omega$ are used interchangeably

$$\omega = 2\pi f$$

The equivalent model with a shorted output and current source applied to the input is shown on the right.

Note: in the following equations, we manipulate the equations until they are in the form s , $1 + s$, etc. Remember that $s = j\omega$

$$V_{b'e} = i_{in} \left(\frac{r_{\pi}}{1 + r_{\pi}(C_{\pi} + C_{\mu}) s} \right)$$

$$i_o \cong g_m V_{b'e}$$


$$i_o \cong g_m i_{in} \left(\frac{r_{\pi}}{1 + r_{\pi}(C_{\pi} + C_{\mu}) s} \right)$$

$$i_o \cong i_{in} \left(\frac{g_m r_{\pi}}{1 + r_{\pi}(C_{\pi} + C_{\mu}) s} \right)$$

But $\beta_0 = g_m r_{\pi}$

$$i_o \cong i_{in} \left(\frac{\beta_0}{1 + \beta_0 \left(\frac{C_{\pi} + C_{\mu}}{g_m} \right) s} \right)$$
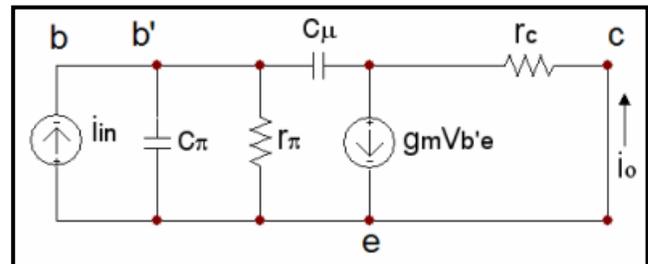
$$\frac{i_o}{i_{in}}(j\omega) = \beta(j\omega) \cong \left(\frac{\beta_0}{1 + \beta_0 \left(\frac{C_{\pi} + C_{\mu}}{g_m} \right) j\omega} \right)$$



At high frequencies, the imaginary component of the denominator dominates. Therefore:

BJT Hybrid Model π

$$\beta(j\omega) \cong \frac{\beta_0}{\beta_0 \left(\frac{c_\pi + c_\mu}{g_m} \right) j\omega}$$

$$\beta(j\omega) \cong \frac{g_m}{(c_\pi + c_\mu) j\omega}$$

$$\beta(j\omega) = 1 \text{ when } \omega = \omega_T$$

$$\omega_T = \frac{g_m}{c_\pi + c_\mu}$$

$$f_T = \frac{g_m}{2\pi (c_\pi + c_\mu)}$$

Common Emitter Amplifier at Low and Mid-band Frequencies

The circuit on the right is a common emitter amplifier using voltage divider bias with a partially bypassed emitter resistor. There is a load R_L , and a source resistance R_s . Note that R_s is the internal resistance of v_s .

After we solve for the quiescent operating point, we are ready to perform calculations for voltage gain and perhaps frequency response. To do so requires us to use a model for the transistor. One model that is typically used is the hybrid model π .

In the circuit on the right, we have the equivalent circuit for the common emitter amplifier shown above. At mid band frequencies, X_{C1} , X_{C2} , and X_{CE} are shorts, but $X_{C\mu}$ and $X_{C\pi}$ are still very large and treated as open. Since X_{CE} is in parallel with R_{E2} , R_{E2} and X_{CE} are both replaced with a short at mid band frequencies.

As discussed earlier, we will assume that the effects of r_b , r_{ex} , and r_o have little effect on the circuit operation due to their value and are removed.

